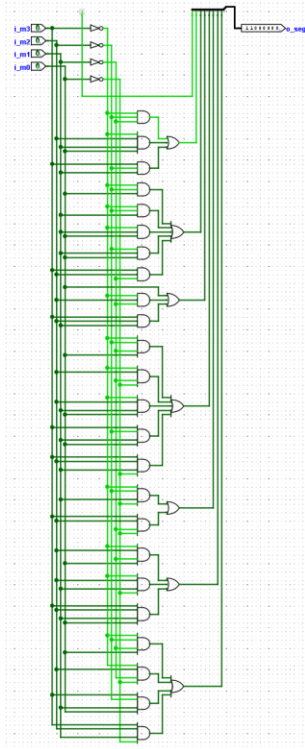



LAB 4 MGM

Segment 7 Decoder

Segment 7 decoder




i_m3	i_m2	i_m1	i_m0	o_seg[7..0]
0	0	0	0	11000000
0	0	0	1	11111001
0	0	1	0	10100100
0	0	1	1	10110000
0	1	0	0	10011001
0	1	0	1	10010010
0	1	1	0	10000010
0	1	1	1	11111000
1	0	0	0	10000000
1	0	0	1	10010000
1	0	1	0	11000000
1	0	1	1	11111001
1	1	0	0	10100100
1	1	0	1	10110000
1	1	1	0	10011001
1	1	1	1	10010010

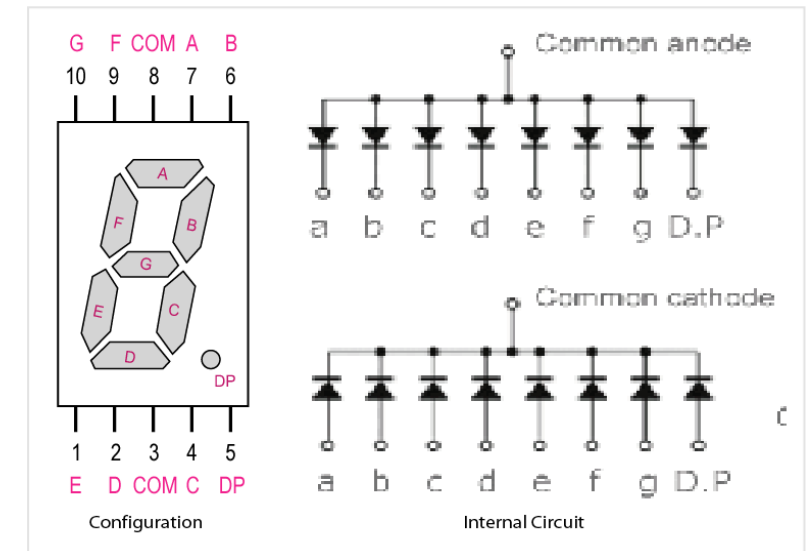

Circuit B

Circuit B

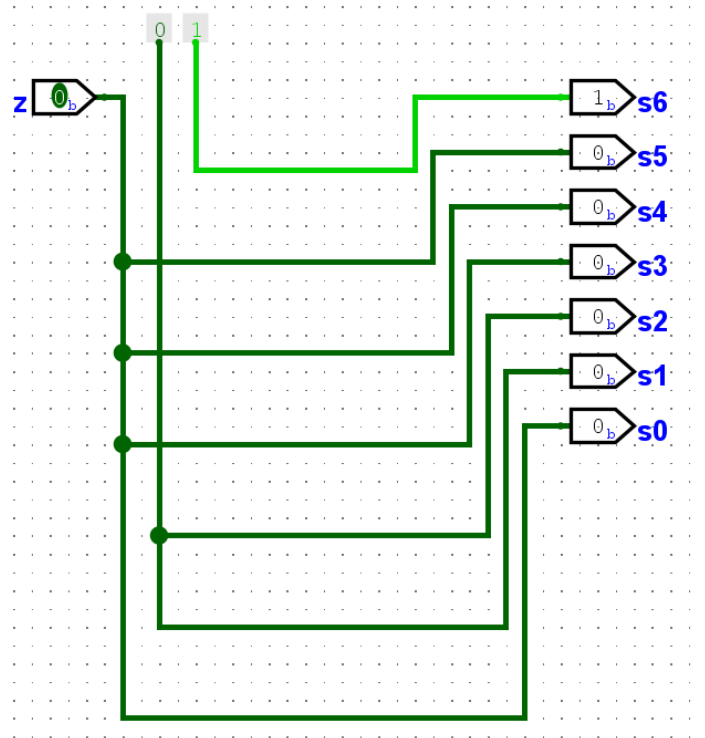


z	s_6	s_5	s_4	s_3	s_2	s_1	s_0
0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	1

MY Comparator

MY Comparator

v3	v2	v1	v0	z
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

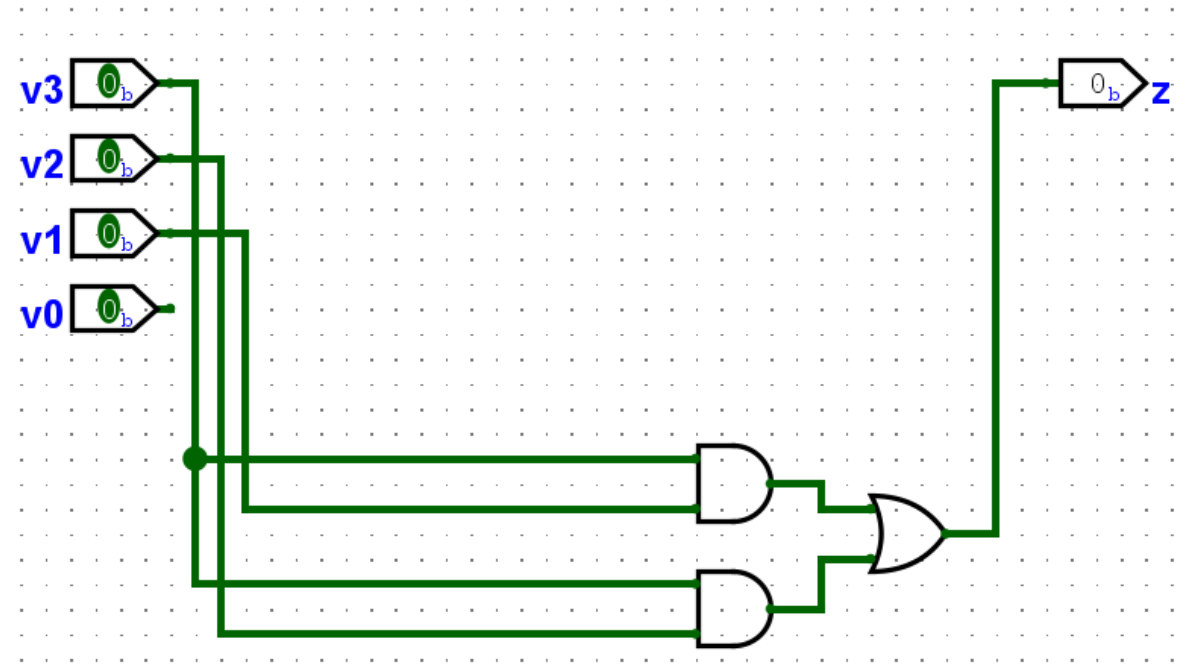

FINAL TEST

FINAL TEST

