

LAB 7

By Mateo GM


Need to fix DownCounter_v1

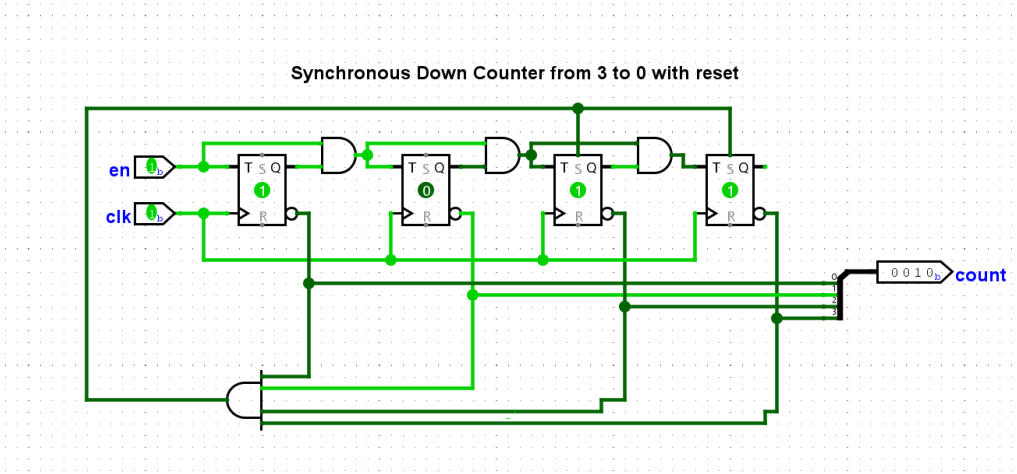Fixed “DownCounter_v1” to count from 3 to 0




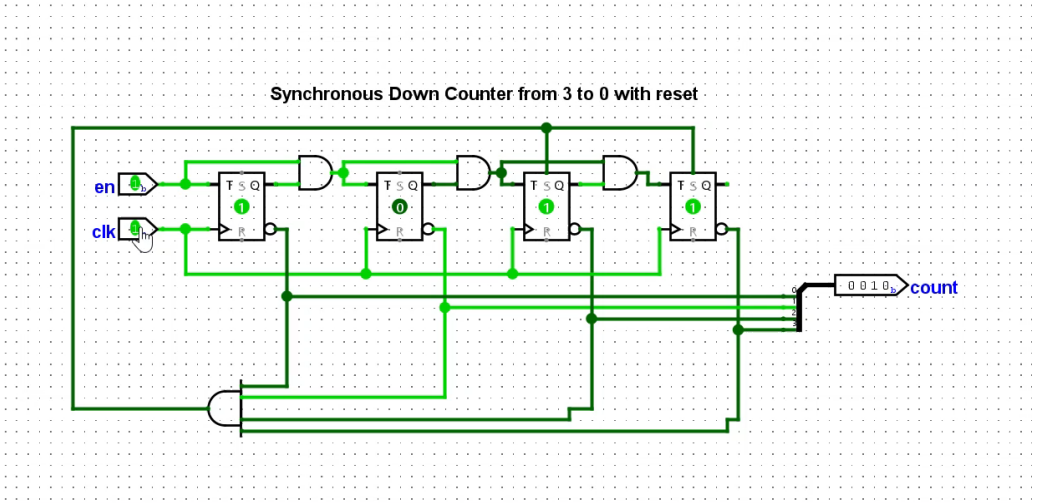


The Design of The FSM Cycle

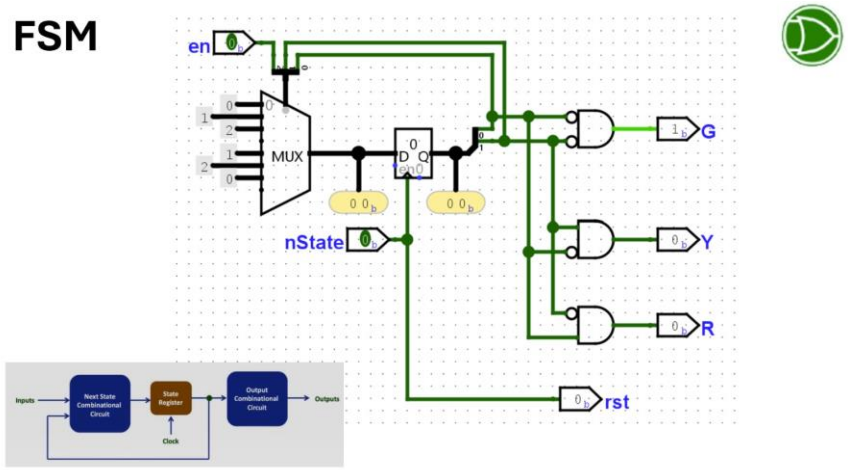

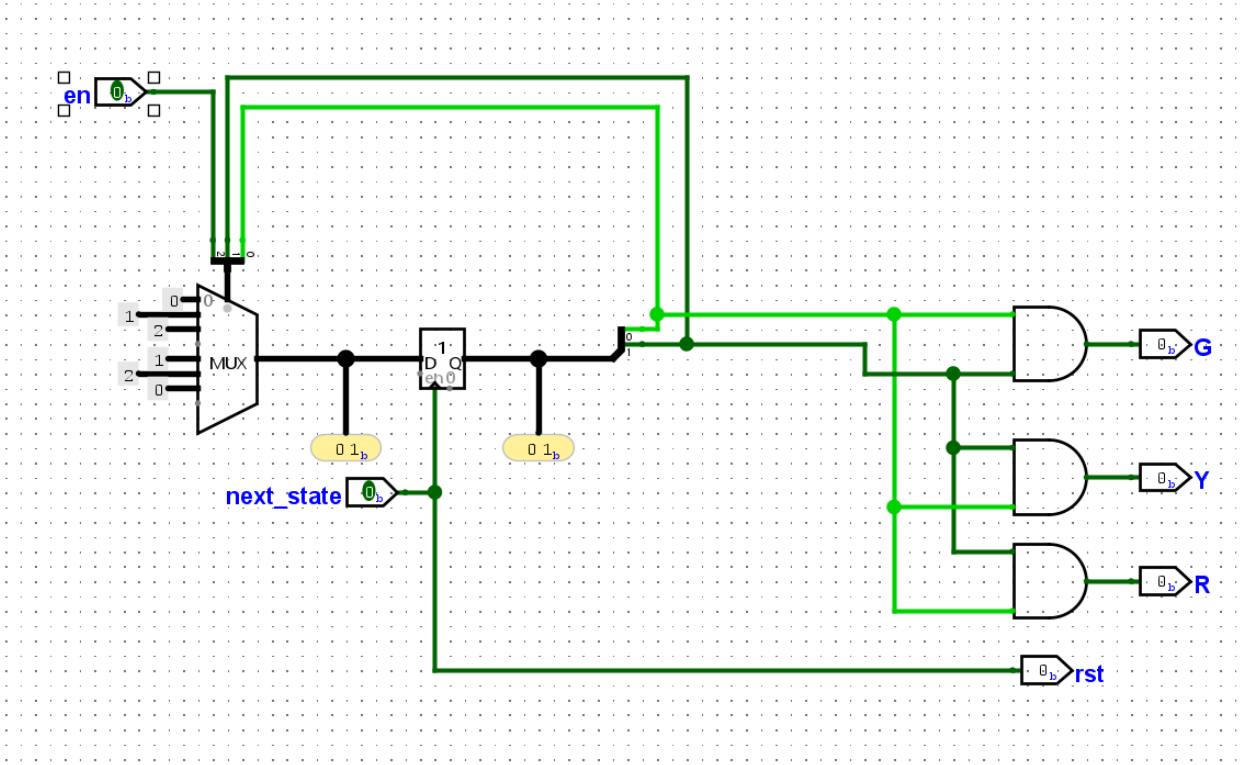Designed the FSM to cycle between Green, Yellow, Red traffic lights



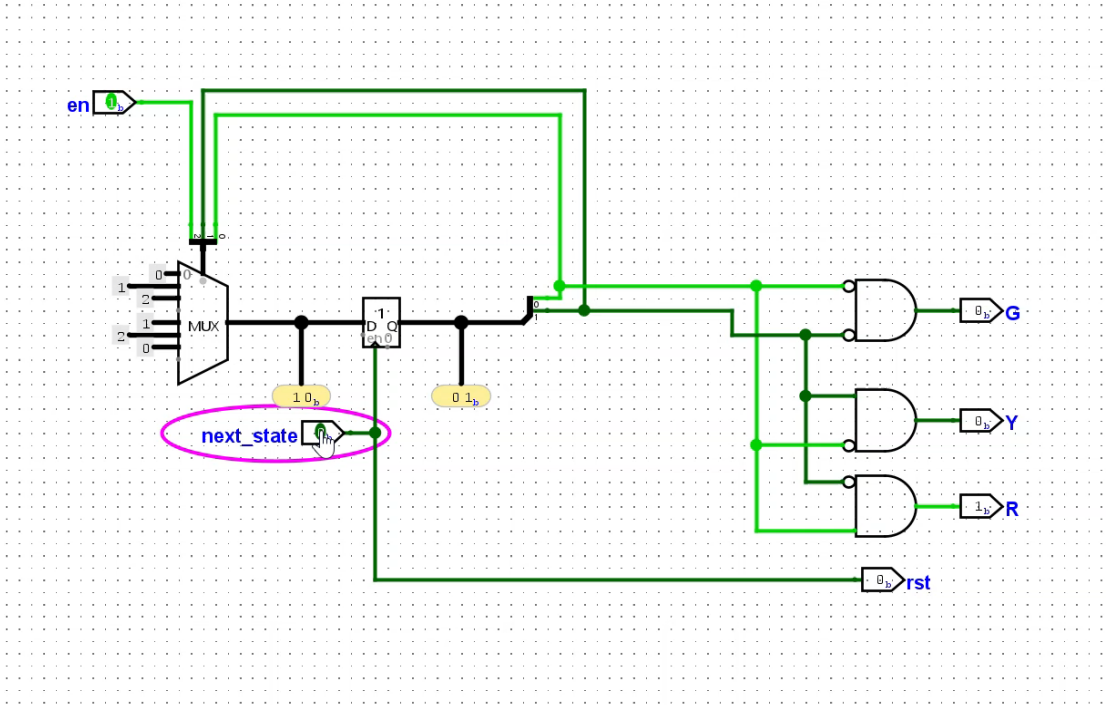

Connected the FSM to the rest of the circuit

