

FINAL PROJECT


By MateoGM

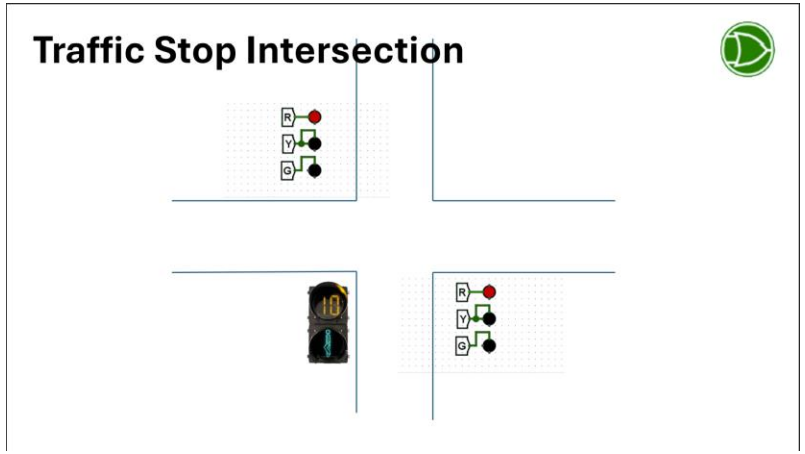


All Gathered Hardware

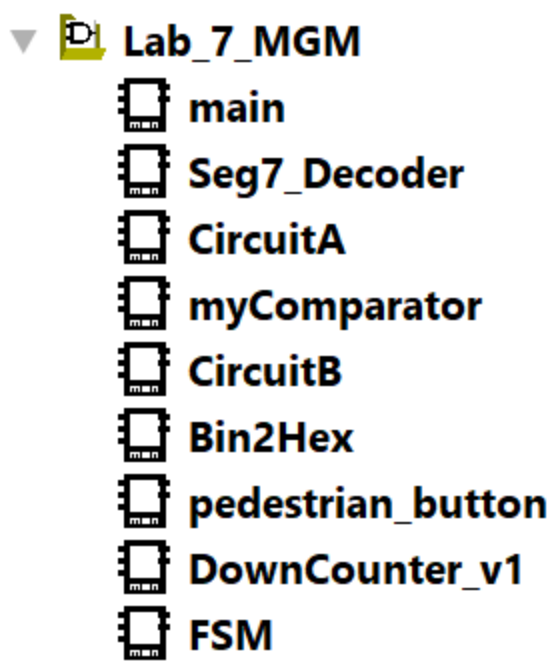All Gathered Hardware for the Traffic Lights:




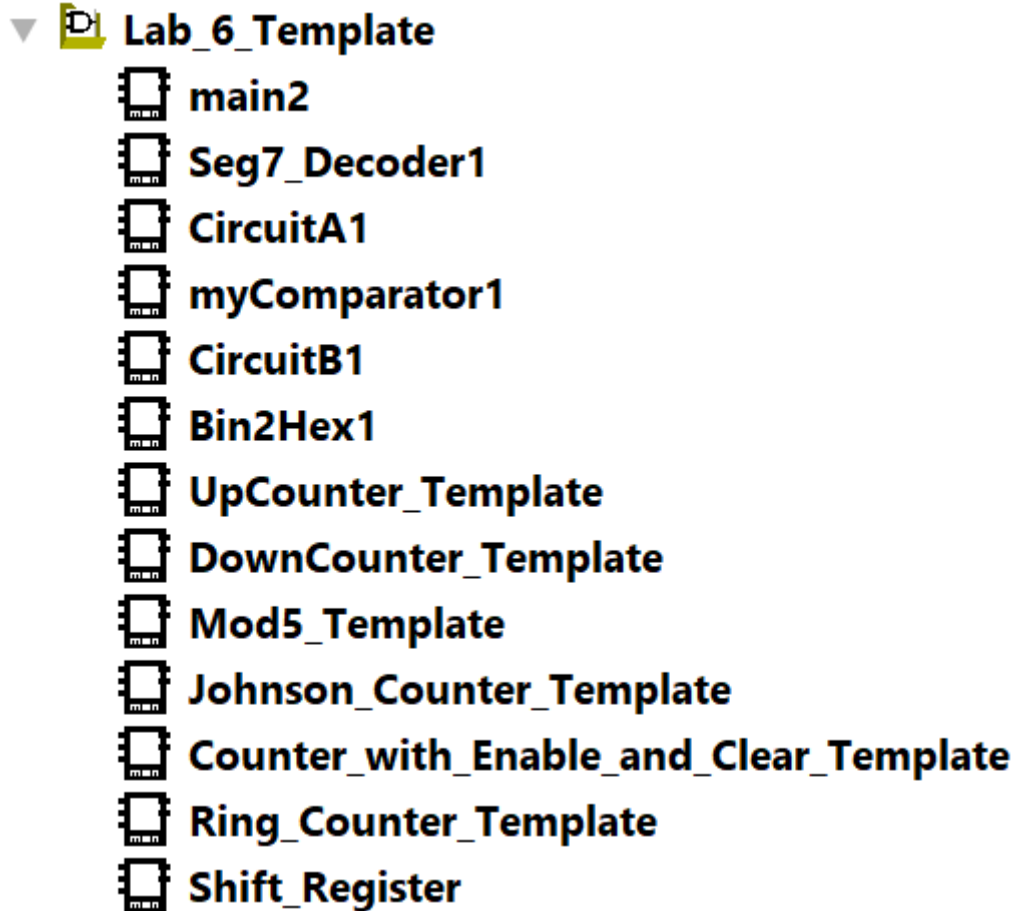

Design of FSM

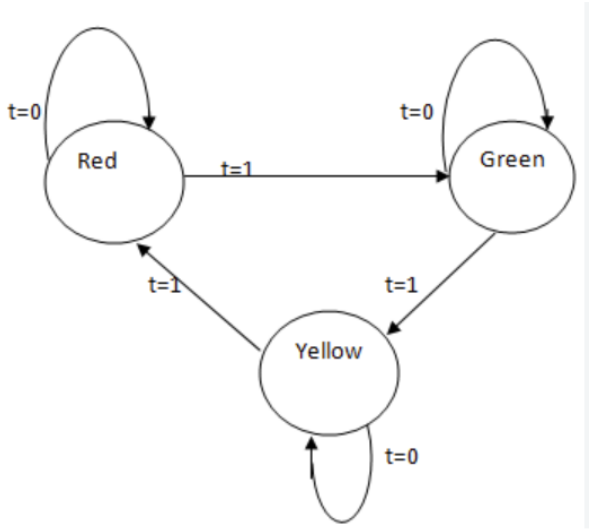


FSM started

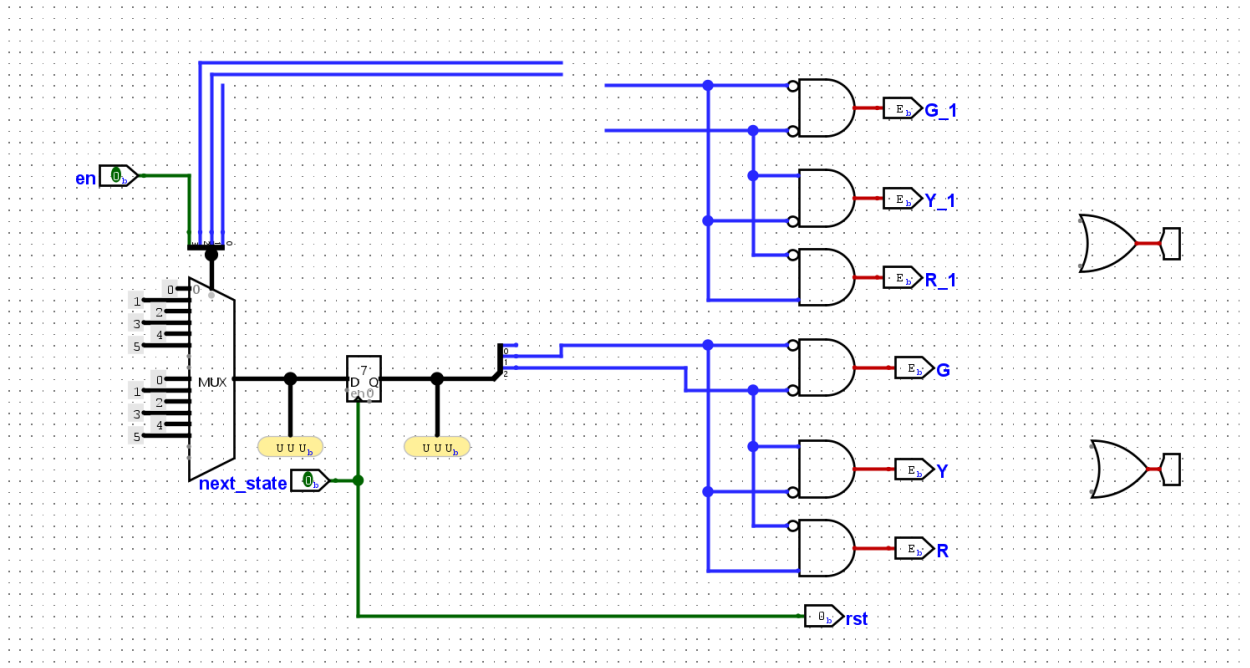


but still contemplating on some solvable solutions for this FSM and trying to implement both Traffic lights into one sole device.


Second chance of the FSM

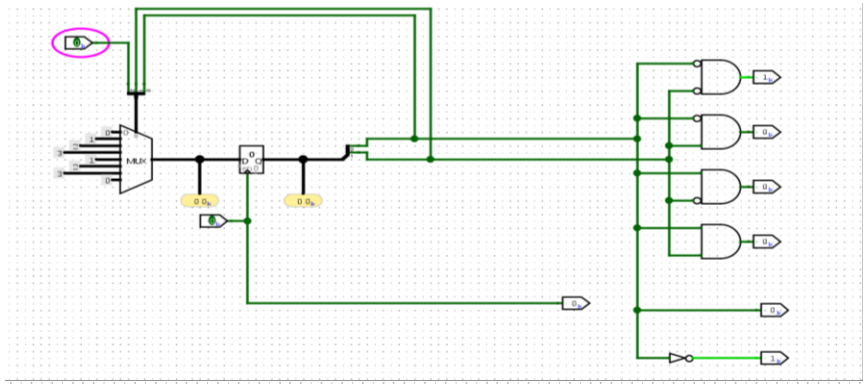

The FSM that
I created

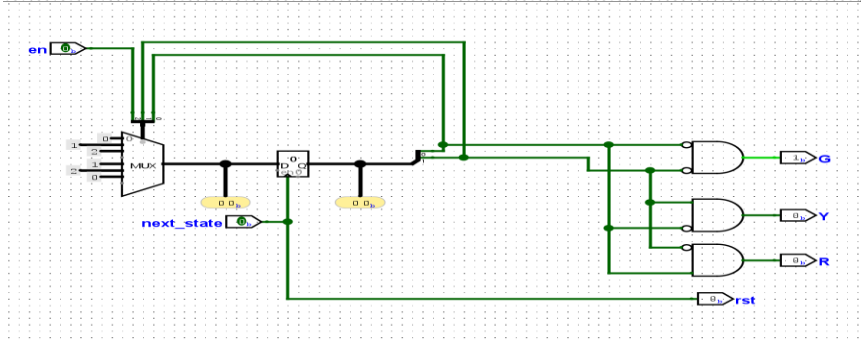



The Original FSM

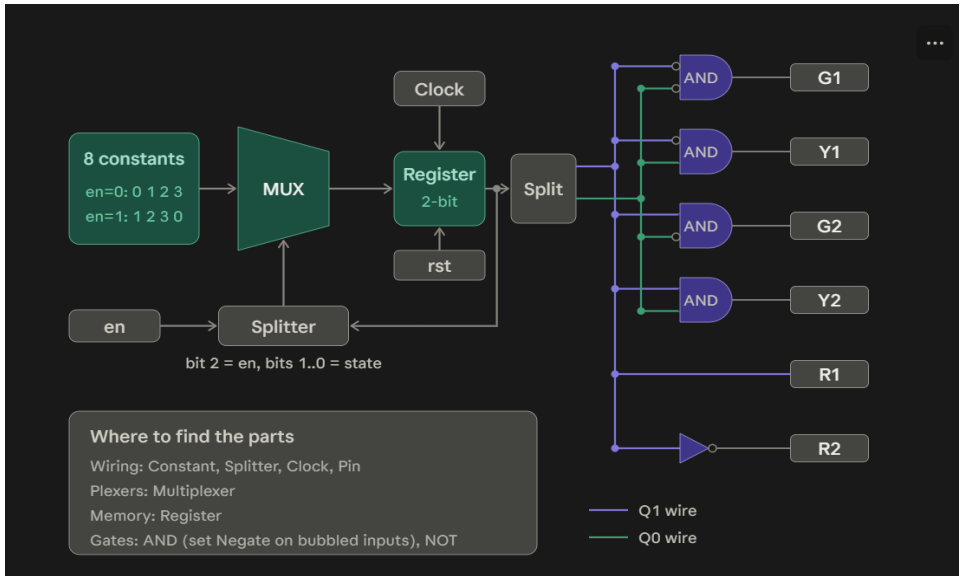

I tried to solve the issue of how to add the AND gates to the main circuit, First I used AI to learn how to implement all the AND Gates into the main function, using that as a stepping stone to understand what to do for the FSM Circuit. I am still fixing a few things, but I used the original circuit we made for the single traffic light as my base.

Third Chance completed full FSM

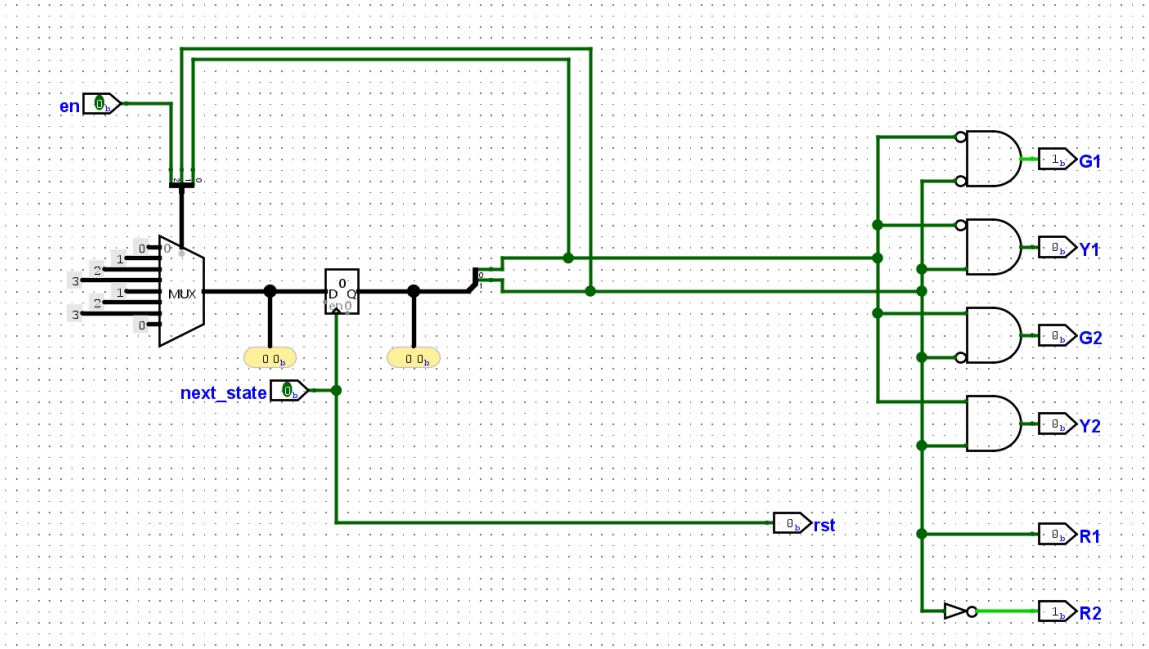


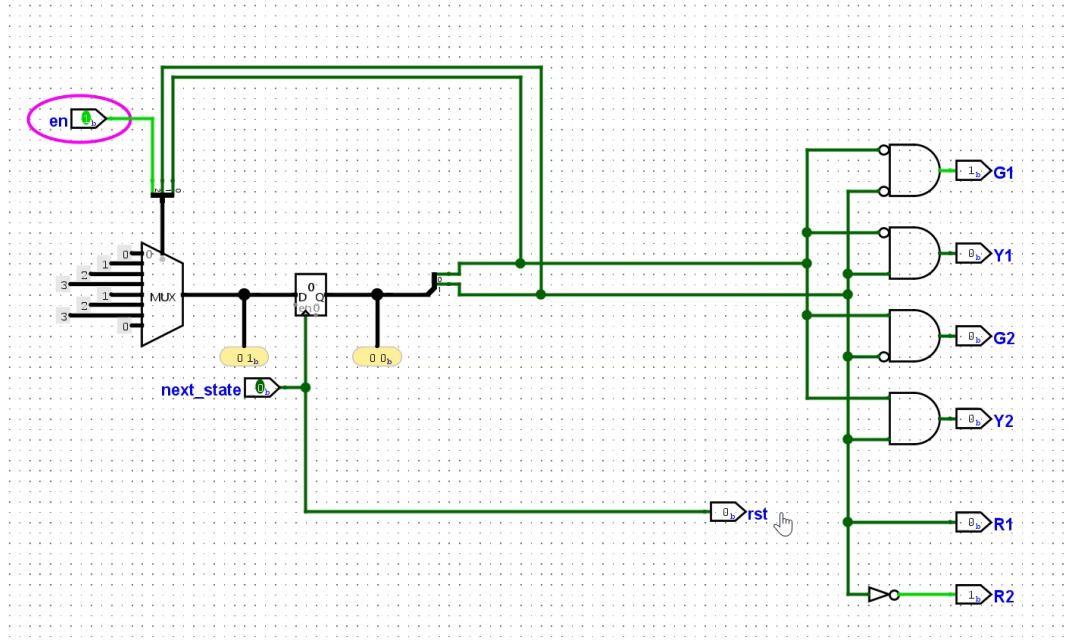


Completed all of FSM and seeing if I fully got it correct

FSM to the Circuit


FSM had a few errors when running

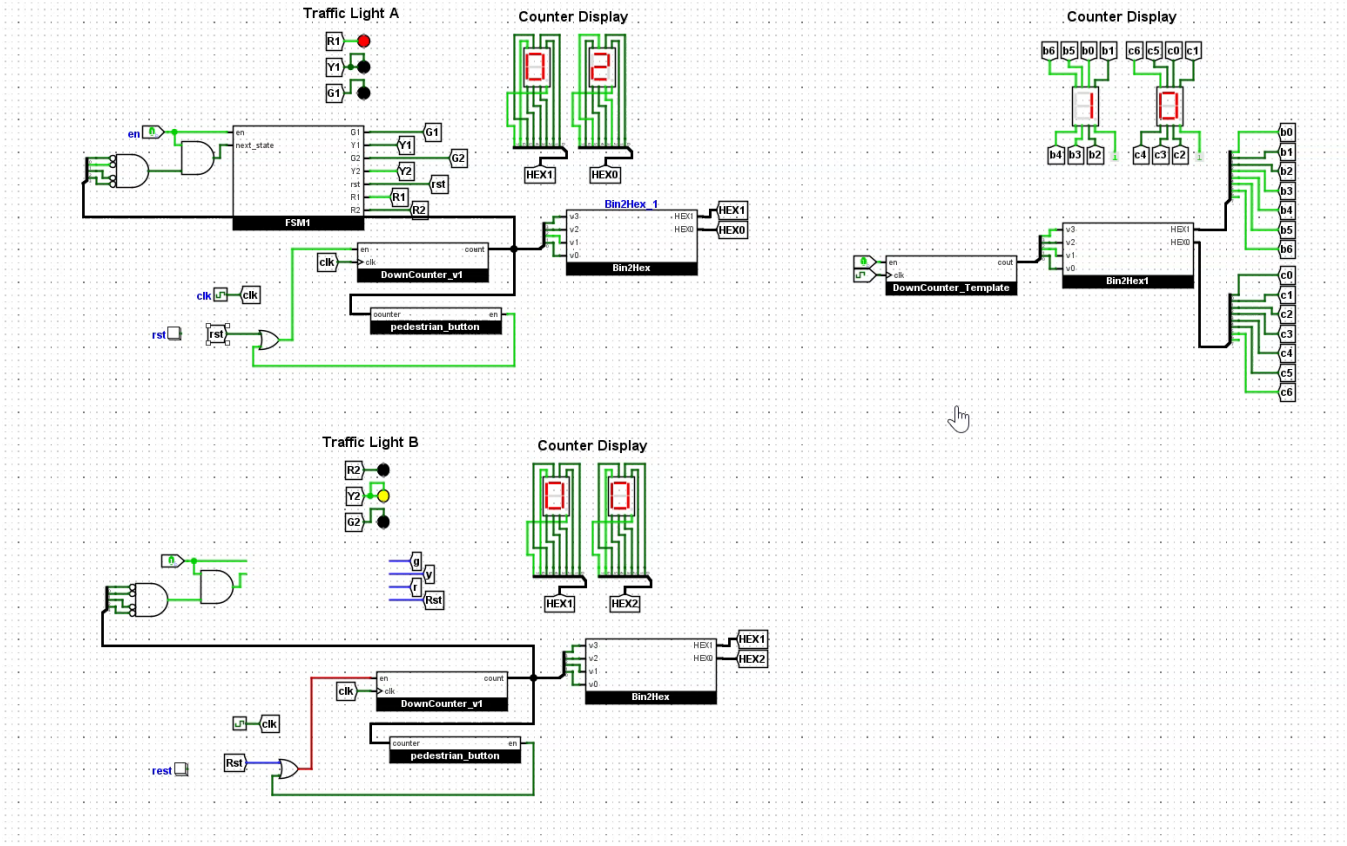

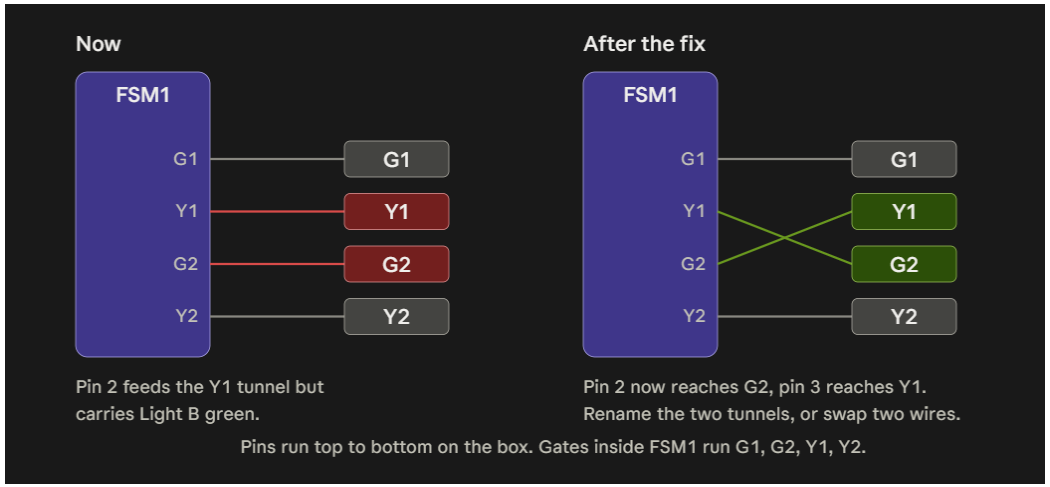

Figured out the problem of the lights and deleted all firmware that was not needed in this project and used AI to help me see what I did wrong and fixed it.

Fixed FSM major errors

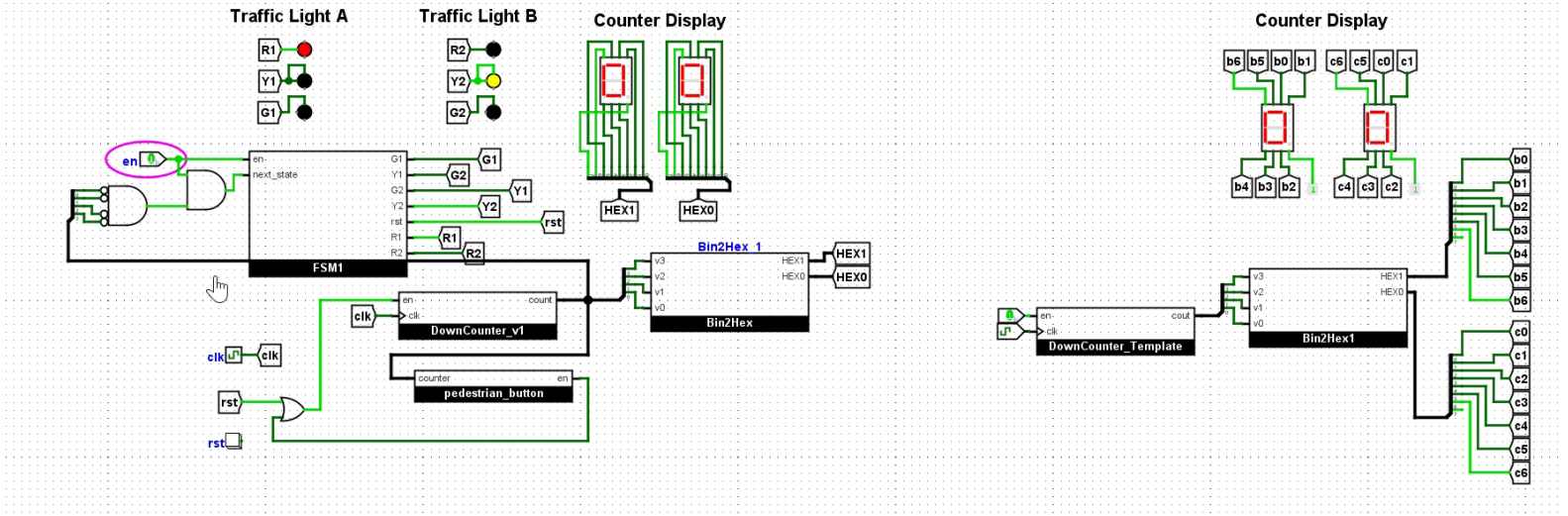

Completed the two traffic lights but still missing the pedestrian button for it to walk about 15 mins. Still in the process.

FSM Completed

Wasn't able to complete the Pedestrian button and 15 min walk, here is what I done:

