

LAB 8


By MateoGM


RGB Circuit

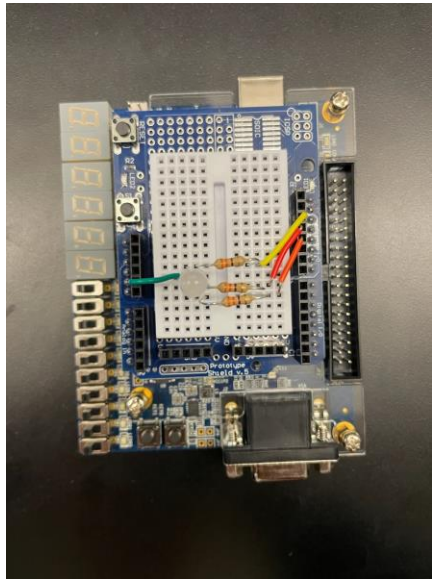

RGB Circuit Completed

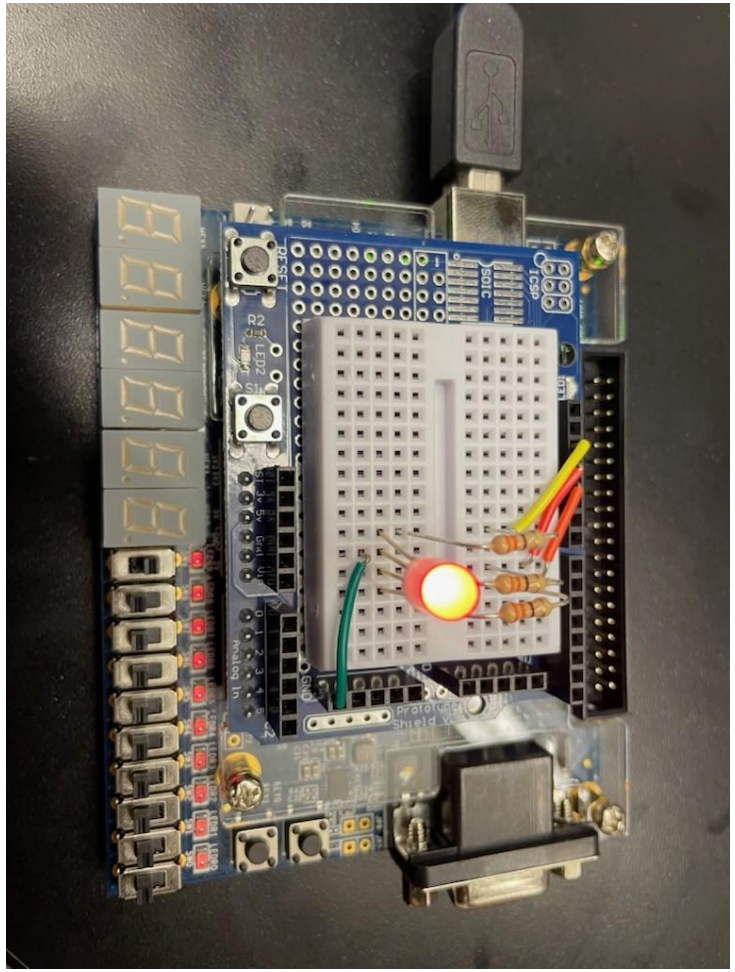


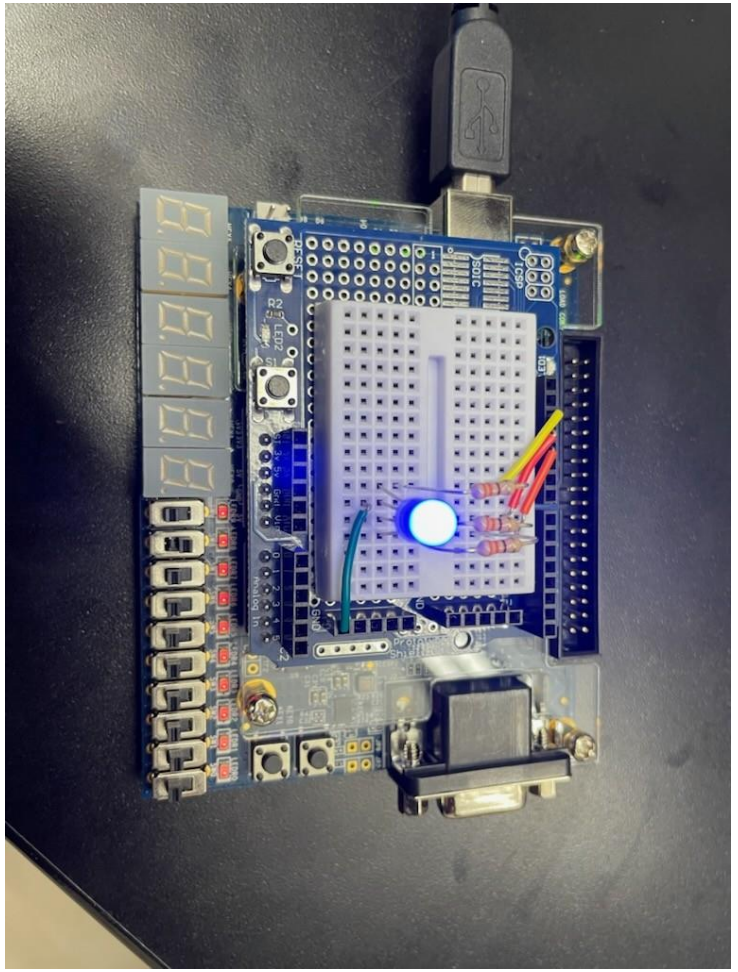


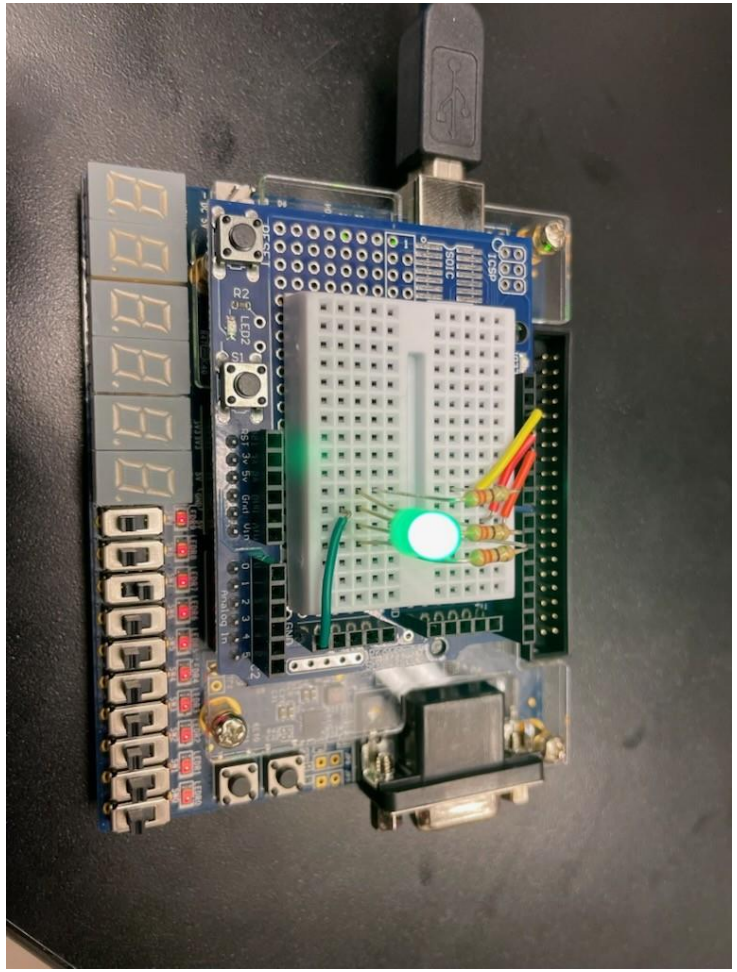


RGB Cycle 8 patterns at 1 sec

My plan A of RGB Cycle

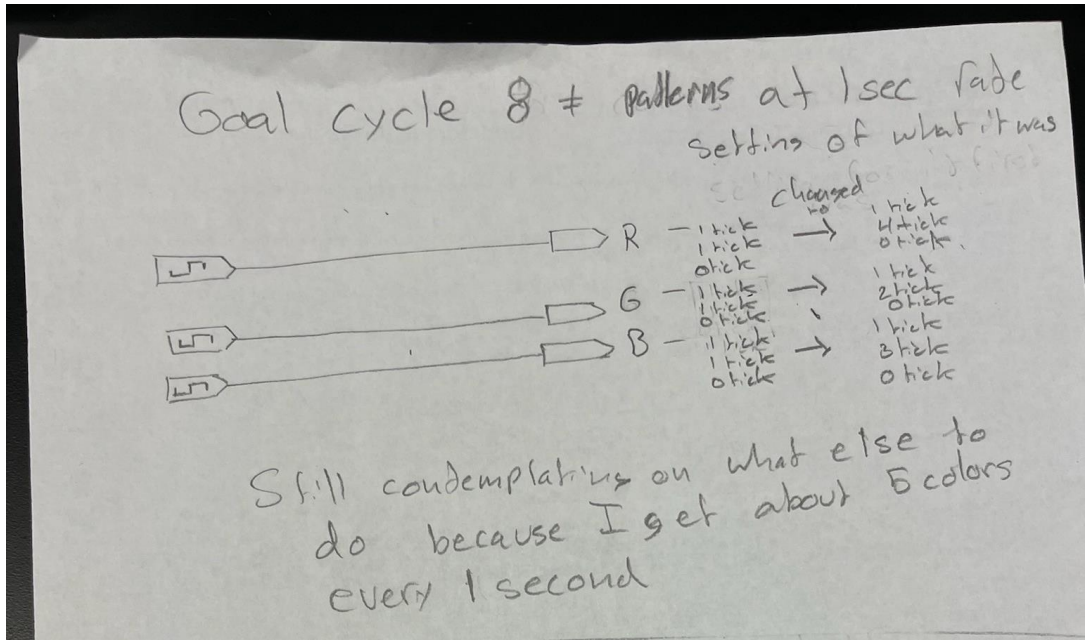

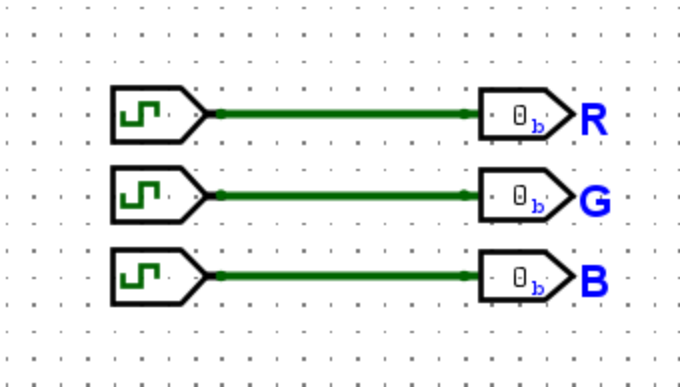


Final Solution:

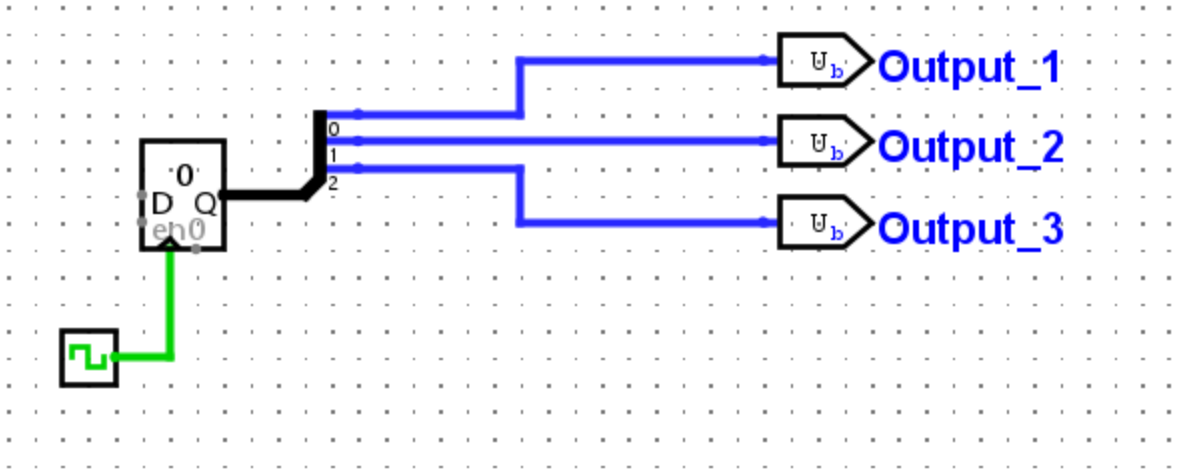

For some reason it's not working for me, and I added all the same things added but for some reason it just doesn't work

RGB Circuit Alternating

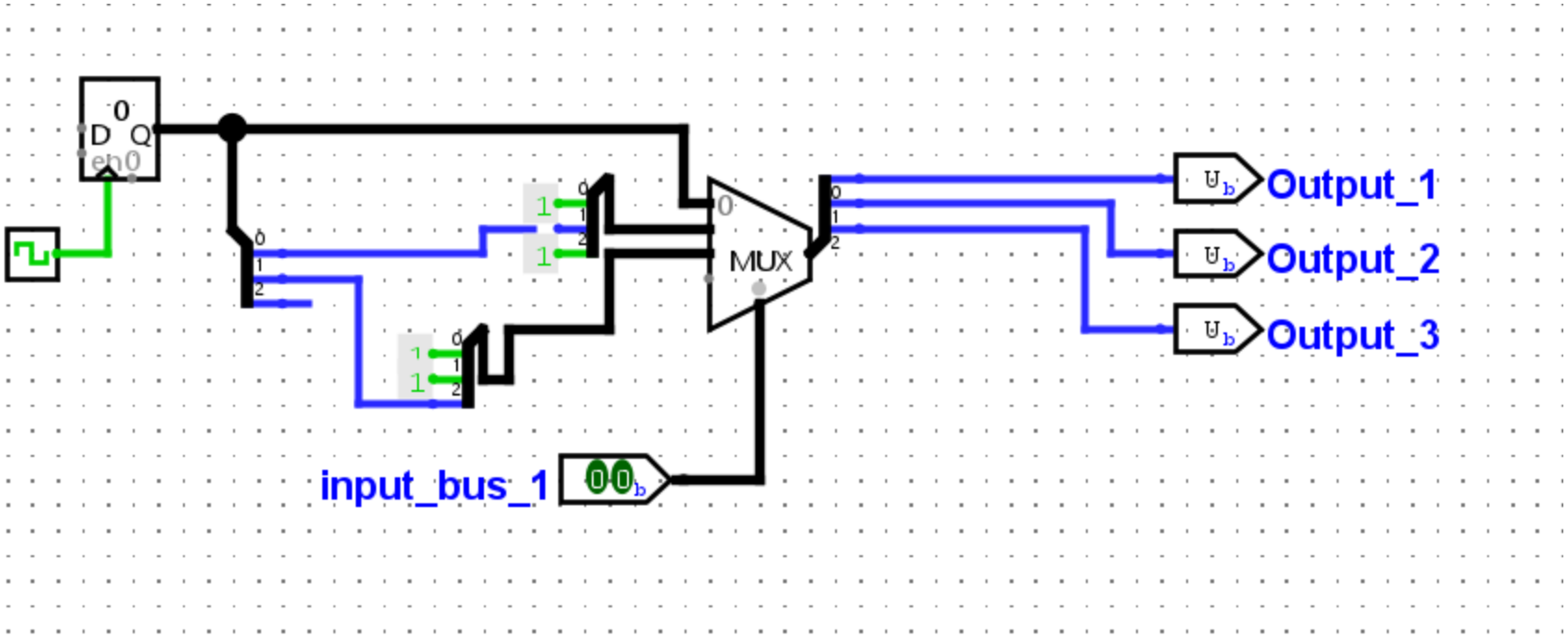RGB Circuit Alternating Function Solution



For some reason it's not working for me, and I added all the same things added but for some reason it just doesn't work